


$$V = V_1 + V_2 \quad R = R_1 + R_2$$

$$V = IR$$

$$V = I(R_1 + R_2)$$

$$V_1 = \frac{R_1}{R_1 + R_2} V$$


* Voltage Division

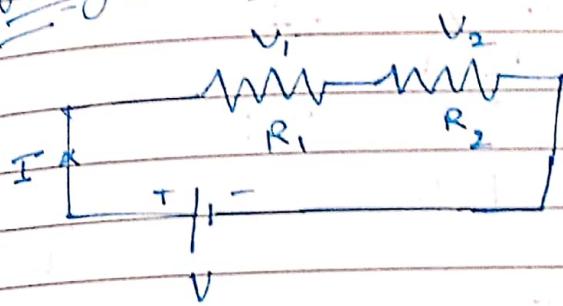

$$V_1 = \frac{R_1}{(R_1 + R_2)} V$$

$$V_2 = \frac{R_2}{(R_1 + R_2)} V$$

* Current Division

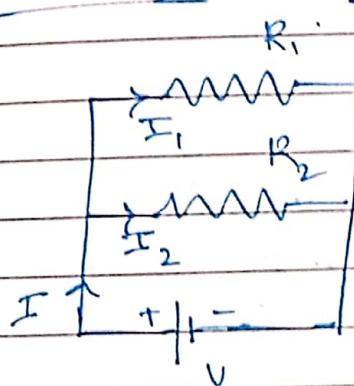



$$I_1 = \frac{R_2}{(R_1 + R_2)} I$$

$$I_2 = \frac{R_1}{(R_1 + R_2)} I$$


Q. Find current in 3 Ω resistance

(a) Using KVL (b) using KCL

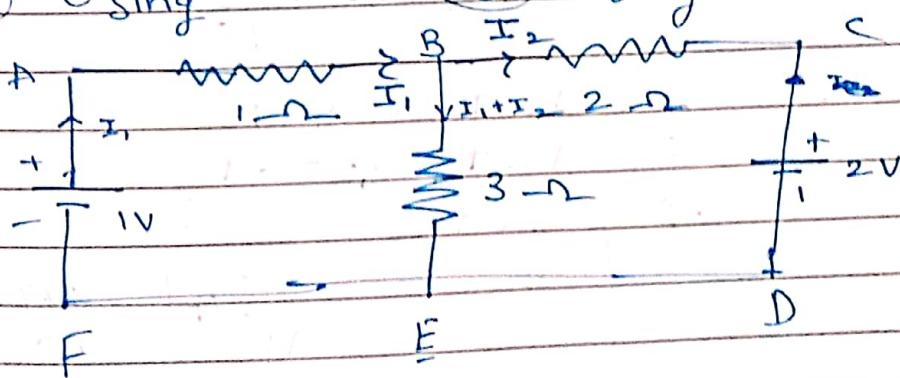

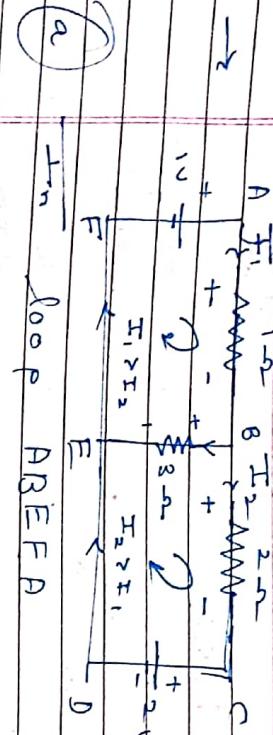

$$I_1$$

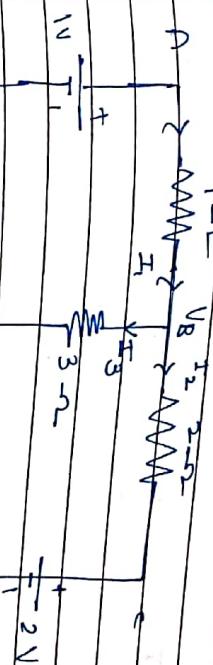

$$I_1$$

DATE _____
NAME _____

APPLY KVL TO CDEF

$$0.2I_3 - 120 + 30R_2 = 0$$

(5)

$$0.2I_3 + 30R_2 = 120 \quad (4)$$

$$0.3I_2 + 20R_1 = 120 - 0.2I_3 \quad (3)$$

- Q. Solve the network for following
 (a) Unknown resistance R_1 & R_2
 (b) Unknown current in varioce
 to branches

$$I_1 = 0.1I_2 - 0.3I_3 - 0.2I_1$$

$$I_2 = 0.3I_1 + 0.2I_3 - 0.1I_2$$



$$\text{From (1)} \quad 20R_1 = 110 - 0.1I_1$$

$$\therefore 0.3I_2 + 0.2I_3 = 120 - 110 + 0.1I_1$$

$$\therefore 0.3I_2 + 0.2I_3 - 0.1I_1 = 10$$

→ Apply KCL to node B & C

$$I_1 = 110 - V_B \quad \therefore I_1 - I_2 = 20 \quad (1)$$

$$0.1I_2 - I_3 - I_2 = 30 \quad (2)$$

Apply KVL to loop ABCGA

$$110 - 0.1I_1 - 20R_1 = 0$$

$$\text{Applying KVL to loop BCFGB} \\ 0.1I_2 - 20R_2 + 20R_1 = 0 \quad (3)$$

$$\therefore 0.3I_2 - 30R_2 + 20R_1 = 0$$

$$\therefore 0.3I_2 + 20R_1 - 30R_2 = 0 \quad (4)$$

$$I_2 = 10 \text{ A}$$

$$I_1 = 10 \text{ A} \quad \therefore I_3 = 40 \text{ A}$$

$$0.1 I_1 + 20R_1 = 110$$

$$+ 20R_1 = 110$$

$$R_1 = \frac{5.95}{0.1}$$

$$0.3 \times 10 + 20 \times \frac{5.95}{0.1} - 30R_2$$



$$\begin{array}{l} R_2 \\ 1 \\ 3 \\ 0 \\ 30 \\ 30 \\ 30 \end{array}$$

$$R_2 = 3.723 \Omega$$

$$R_2 = 60.1 \Omega$$

$$R_2 = 3.723 \Omega$$

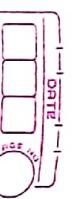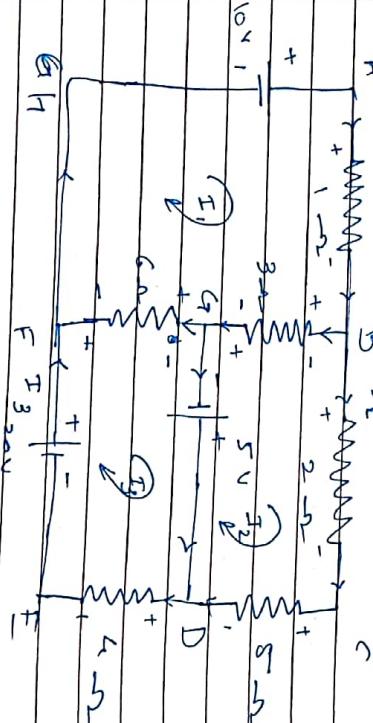Find current in R_2 & 6Ω resistor for
using KVL



Apply KVL to ABGFHA

$$-I_1 - 3(I_1 - I_2) - 6(I_1 - I_3) + 10 = 0$$

$$-I_1 - 3I_1 + 3I_2 + 6I_1 - 6I_3 = 10$$

$$10 = 10I_1 - 3I_2 - 6I_3 \quad (1)$$

Apply KVL to BCDFG

$$-2I_2 + 5I_2 + 5 + 3I_2 - 3I_1 = 0$$

$$2I_2 - 3I_1 = -5 \quad (2)$$

Apply KVL to GDEFHG

$$-10I_2 - 3I_1 = -5 \quad (3)$$

$$3I_1 - 10I_2 = 5 \quad (2)$$

From (2) & (3) & (3)

$$I_1 = \frac{5 + 10I_2}{10} \quad I_2 = \frac{3I_1 - 5}{10}$$

$$I_2 = \frac{25 + 6I_1}{10} \quad \text{in (1)}$$

$$10 = 10I_1 - 3(\frac{3I_1 - 5}{10}) - 6(\frac{25 + 6I_1}{10})$$




$$10 = 10 + -9T_1 + 15 - 75 - 18T_1$$

$$100 = 100T_1 - 9T_1 + 15 - 150 - 36T_1$$

$$\therefore 250 - 15 = 100T_1 - 45T_1$$

$$235 = 55T_1$$

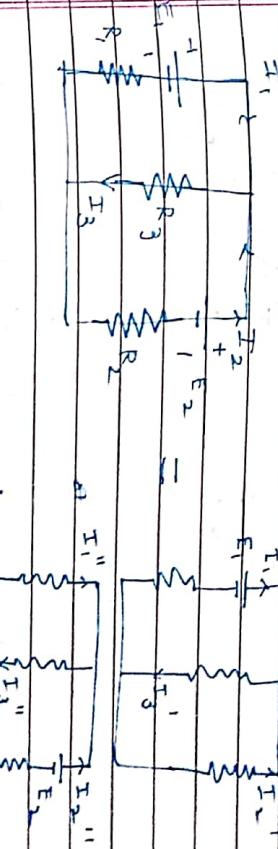

* Superposition Theorem :-
A linear network containing more than one source of emf resultant current in any branch algebraic sum of the currents that would have been produced by each source of emf taken separately (with all other sources of emf being replaced by their respective internal resistance)

*

Thevenin's Theorem :-

Any two terminals of network can be replaced by an equivalent voltage source and equivalent series resistance A voltage source is voltage across two terminals with load removed. Series resistance is the resistance of network measured between two terminals with load removed and constant voltage sources being replaced by that internal resistance.

$$I_3 = 25 + 6 \times 4.27$$

$$10$$

$$E_0 = 5.662 \text{ V}$$


$$T_{\text{load}} R_2 = I_1 + I_3 = 1.27 - 5.66$$

$$= -0.79 \text{ A}$$

$$= 0.79 \text{ A from FBD}$$

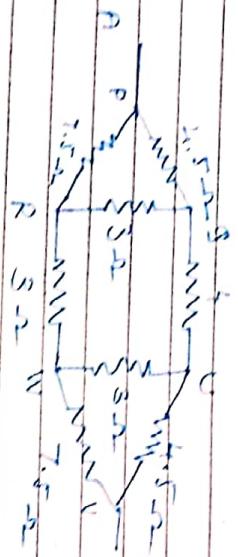a. Find an equivalent resistance betn A & G


$$0.9 + 4 + 0.9 = 5.8$$
$$1.5 + 3 + 1.5 = 6$$
$$6 \parallel 4$$



$$0.25 + 0.25 + 2.4$$
$$0.5 + 2.4 = 2.9$$


Converges to a value in star

b. Find equivalent resistance betn P & Q

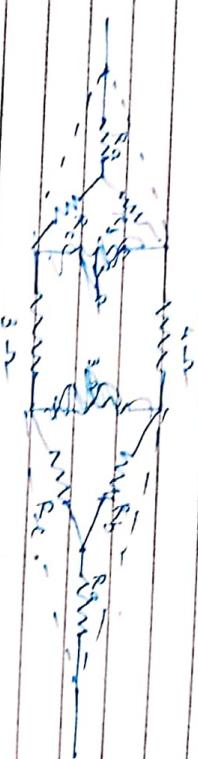

Find equivalent resistance betn P & Q
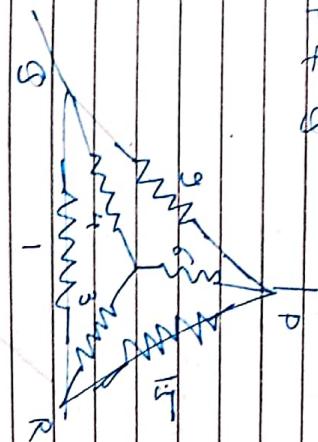
$$R_P = 4.5 + 7.5 = 12$$
$$4.5 + 7.5 + 0 = 12$$
$$" = 12$$
$$" = 12$$
$$" = 12$$
$$" = 12$$
$$" = 12$$



$$R_Q = 2.25 + 0.9 + 2.25$$
$$2.25 + 0.9 = 3.15$$
$$3.15 + 2.25 = 5.4$$
$$5.4 + 1.5 = 6.9$$
$$6.9 + 2.25 = 9.15$$


$$R_Q = 13.5 + 1.5 = 15$$
$$15 + 2.5 = 17.5$$
$$17.5 + 2.25 = 19.75$$
$$19.75 + 1.5 = 21.25$$
$$21.25 + 2.25 = 23.5$$

$$\mu_{NS} = 1.62$$

it is similar to

* Magnet

* Electrical ckt

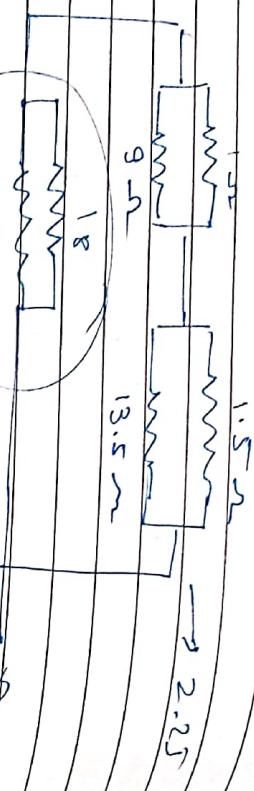

Magnetic flux = imaginary lines indicate direction of magnetic field is called magnetic flux, unit (wb)



1) It is defined as maf required to circulate flux through unit length ($A.T/m$) $\frac{N \cdot I}{L} = H = mmf/L$

$$= \frac{1}{6} + \frac{1}{2.25}$$

2) It is space which circulates magnetic flux in the magnetic ckt (A.Turns)

* Magnetic circuits :-

magnetic flux (ϕ)
magn. flux density (B)
magn. field strength (H)
magnetic force (mmf)
Absolute permeability (μ_0)
Reluctance (σ)

σ is ratio of magnetic flux density to magn. field strength
 $\mu = \frac{B}{H}$, $\sigma = \frac{1}{\mu}$

3) It is opposition of magnetic ckt to passage of magn. flux through it

$$R = \frac{\mu \cdot l}{A}$$

$$S = \frac{\mu \cdot maf}{H}$$

Similarities



Elec CLK +

magn. ckt

Relation b/w electric f-th.

2) Emf in coil 2) mmf ip ∂T

3) $\frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$

1. $\frac{d}{dt} \int_{\Omega} u^2 dx = -2 \int_{\Omega} u_t u dx$

11
11
11

4

Diferente de todos

Heat - Barrier of Proprietary

卷之三

relation betw. elec. f mech. energy

11 36 males

Relation betw. thermo & m - l - t -

$$H_{\text{ref}} = \text{mechanical} \quad 1 \text{ cal} = 4.187 \text{ Joule}$$

of heat (J)

$$\therefore 0.25 \times 860 = 215 \text{ kcal}$$

$$B_1 = \{x \in \mathbb{R}^n : \|x\|_2 \leq 1\}$$

215 " 4 (42) 10

卷之三



* A heater takes 1 hour to heat 50 kg of H_2O from $20^\circ C$ to Boiling point calculate

elect. energy in kWh of power rating

\rightarrow

$$\alpha = ms \Delta \theta$$

$$\alpha = 50 \times 1 \times (100 - 20)$$

$$\alpha = 4000 \text{ k cal}$$

$$\alpha = \frac{4000}{860 \times 10^3} \text{ cal}$$

$$\alpha = 4.65 \text{ kWh}$$

$$(\text{Elec. energy})$$

$$\text{power rating} = \frac{E}{t} = \frac{465 \text{ kWh}}{1 \text{ hr}}$$

Magnetic saturation :-

$$\rightarrow mmf \uparrow = B \uparrow$$

- limit for increase in B in magnetic field

- highest reluctance



\rightarrow saturation - Beyond limit, no good conductor of flux

- so more mmf to develop flux in core


\star

Magnetic leakage flux :-

- Follows a path not intended for it


$$mmf = \frac{\Delta \theta}{\alpha}$$

$$S = mmf = \frac{l}{\alpha}$$

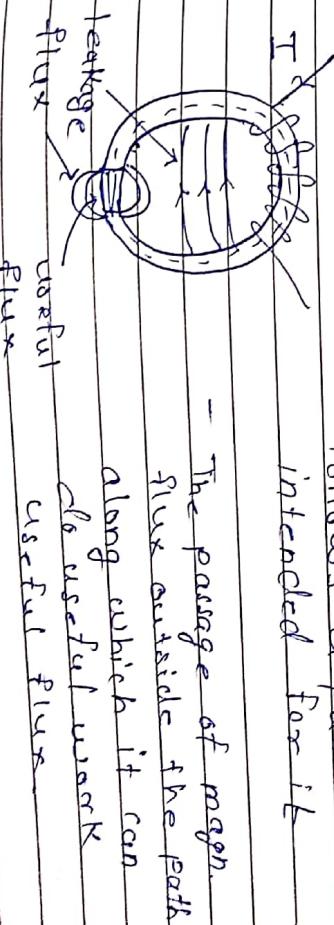

$$H = \frac{N \cdot I}{l}$$

$$B = \mu_0 \cdot H$$

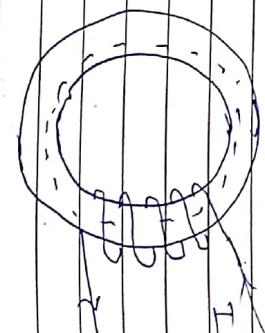

$$B = \mu_0 \frac{NI}{l}$$

$$\text{Leakage flux} = \frac{\text{Total (leak + useful) flux}}{\text{Useful flux}}$$

$$\phi = B \cdot A = \text{Magnetic flux} = NI$$

$$\frac{\phi}{A} = \frac{NI}{l} = \frac{m.m.f}{l}$$

$$\frac{\phi}{A} = \frac{NI}{l} = \frac{m.m.f}{l}$$

R-L-C Series

$$i) V_L > V_R$$

$$ii) V_L < V_R$$

$$iii) V_L = V_R$$

∴



$$V_L = V_R + V_C$$

$$= V - X_L - X_C$$


$$= V \left(\frac{1}{X_L} - \frac{1}{X_C} \right) = V/X$$

$$I = I_R + j(I_I_L - I_C)$$

$$\text{where } |I_L - I_C| = I_X$$

$$I^2 = \sqrt{I_P^2 + I_X^2} = \sqrt{\frac{V^2}{R^2} + \frac{V^2}{X^2}} = \frac{V}{Z}$$

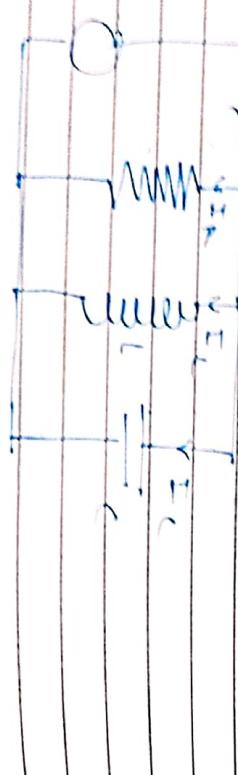Two sinusoidal currents are given as
 $I_1 = 10\sqrt{2} \sin(\omega t + 60^\circ)$
Find expression for sum of these currents



$$I_R = \frac{V}{R}, \quad I_L = \frac{V}{X_L}, \quad I_C = \frac{V}{X_C}$$

$V_R = V_L = V_C = V$ (Supply voltage)

$$\begin{aligned} I_R &= \frac{V}{R}, \quad I_L = \frac{V}{X_L}, \quad I_C = \frac{V}{X_C} \\ I &= (10, 60^\circ) + (20, 160^\circ) \\ &= (10 + j(10)) + (10 + j(17.32)) \end{aligned}$$

$$= 20 + (17.32)j \quad \theta = 40.8^\circ$$

$$H_3 = H_2 \times \frac{1}{2}$$

$$H_3 = 37.5 \times \frac{1}{2}$$

$$H = 37.5 \sin(37.5t + 45^\circ)$$

$$\text{Vavg} = \frac{2V_m}{\pi} = \frac{40}{\pi} = 12.73 \text{ V}$$

$$\text{Reactance} = \frac{H_3}{I} = \frac{2 \times 7}{\pi} = 4.456 \text{ N}$$

$$X_{avg} = \frac{V}{I} = \frac{20}{2} = 10 \text{ N}$$

$$T_{avg} = \frac{H}{P} = 10 / 4.456$$

$$\text{Impedance} = \frac{V_m}{I} = \frac{20}{7} = 2.857 \text{ N}$$

$$\text{Power Factor} = \cos \phi = \cos 60^\circ = 0.5 (\text{Lead})$$

$$P_{avg} = 20 = 50$$

$$(2) \quad 2 = \angle 36.85^\circ \quad x = 17.6, y = 13.19$$

$$17.6 + 13.19j$$

(3)

$$P(15, 10) \rightarrow 70.17 \angle 85.9^\circ$$

Multiplication in Polar Form

$$A = (10 \angle 20) \text{ N}$$

$$B = (30 \angle 80) \text{ N}$$

$$A \times B = (10 \times 30) \angle (20 + 80)$$

$$A/B = (10/30) \angle (20 - 80)$$

$$\text{Active Power} = V_{avg} \times I_{avg} \cos \phi$$


$$= 69.998 \times \frac{1}{2}$$

$$= 34.99 \text{ W}$$

Time taken b/w max value & next zero value

$$t = \frac{1}{f}$$

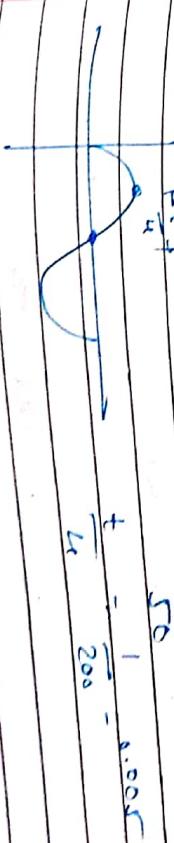- i) Ind. i) Avg Value of V & I of current
- ii) RMS of V & I of current
- iii) Impedance
- iv) Power factor
- v) Active power
- vi) Power



Ques

Ans



Q. 2) 

$$= 5.834 \angle (+28.9^\circ) A$$

$$Z_1 = R_1 + jX_L$$
$$= 5.834 L 28.9^\circ (10 + j(15.11))$$
$$= 5.834 L 28.9^\circ \times 15.62 \angle 57.5^\circ$$

Draw vector diagram for ckt shown indicating terminal vts V_1, V_2 & current also calculate current through ~~at~~ ckt V_1, V_2 & power factor

$$X_L = 2\pi f L$$

$$X_{L1} = 2\pi \times 50 \times 0.05$$

$$X_{L2} = 31.4 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$X_C = 63.69 \Omega$$

$$R_1 = 10 \Omega, R_2 = 20 \Omega$$

$$Z = \frac{V}{I} \therefore I = \frac{V}{Z}$$

For this ckt

$$Z = R_1 + R_2 + jX_L + jX_C - jX_C$$

$$Z = 30 + j(-16.59)$$

$$Z = 30 - j(16.59)$$

$$I = \frac{V}{Z} = \frac{200}{30 - j(16.59)}$$

$$\therefore V_2 = I Z_2$$


$$= 5.834 L 28.9^\circ \times (20 - 32.29j)$$
$$= 5.834 L 28.9^\circ \times 37.98 \angle -58.2^\circ$$
$$= 221.57 L - 29.3^\circ$$

Power Factor = $\cos \phi$

$$= \cos(28.9^\circ)$$
$$= 0.875 W \text{ consumed leading}$$

vector diagram



leading

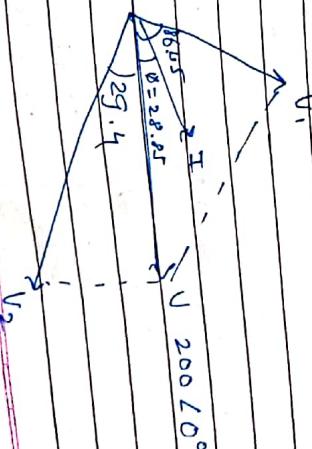

Q3

A reactor having negligible resistance inductance of 0.1H is connected in series with resistor of 15 ohm . The circuit is connected across $230\text{V}, 50\text{Hz}$ single phase AC supply calculate i) current in ct ii) power factor iii) v/tg place resistor & load factor

$$R = 15 \Omega \quad L = 0.1\text{H}$$

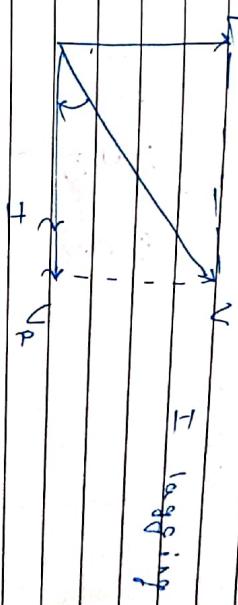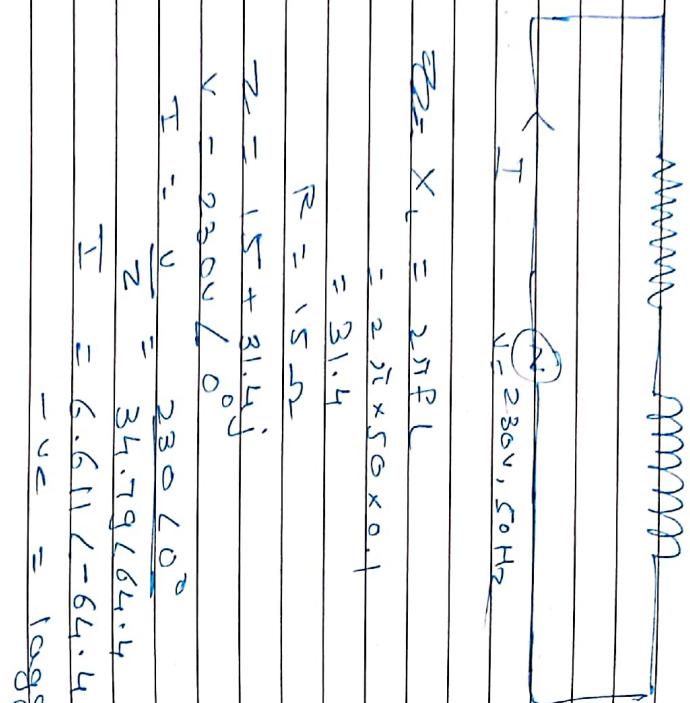

Q3 A capacitive reactance of 4Ω is connected in series with resistors of 5Ω . If $230\text{V}, 50\text{Hz}$ calculate i) capacitance, impedance, supply current, V/tg drop, capacitive power factor, reactive, active & apparent factor.

$$\begin{aligned} X_C &= \frac{1}{2\pi f C} \\ &= \frac{1}{2\pi \times 50 \times 0.1} \\ &= 31.4 \Omega \\ R &= 15 \Omega \\ Z &= 15 + 31.4j \\ V &= 230 \angle 0^\circ \\ I &= \frac{V}{Z} = \frac{230 \angle 0^\circ}{34.79 \angle 64.4^\circ} \\ I &= 6.611 \angle -64.4^\circ \\ -V_C &= \text{lagging} \end{aligned}$$

$$\text{power factor} = \cos(64.4^\circ)$$

$$= 0.4320$$

$$\begin{aligned} V_A &= I \times R \\ &= 6.611 \angle -64.4^\circ \times (15 \angle 0^\circ) \\ &= 6.611 \angle -64.4^\circ \times (31.4 \angle 0^\circ) \\ &= (6.611 \angle -64.4^\circ) \times (31.4 \angle 90^\circ) \end{aligned}$$

$$V_L = 207.58 \angle 25.6^\circ$$

$$V_A = I \times R$$

$$= (6.611 \angle -64.4^\circ) \times (15 \angle 0^\circ)$$

$$= 99.165 \angle -64.4^\circ$$

* Phase voltages:

1) Voltage generated in each phase winding is called phase voltage

Ex. V_A , V_B

2) Current supplied by each phase is phase current. Ex. I_A

* Line voltage

Line voltage = voltage available between any two lines of system. Ex. V_{AB}

2) Line current = current passing through line. Ex. I_B

* Star connection

$$E_{line} = \frac{1}{\sqrt{3}} E_{phase}$$

* Delta connection

$$\rightarrow \text{Lap : } A = P(\text{pole}) \quad E_g = 400 \text{ V}$$

$$\text{wane : } A = 2 \quad N = 1000 \text{ rpm}$$

$$Z = 80 \times 10 = 800$$


(no of conductors)

$$E_g = \frac{\Phi Z N F}{60 A} \quad (A = P)$$

$$E_g = \frac{\Phi Z N F}{60 A} \quad (A = P)$$

$$E_g = \frac{\Phi \times 800 \times 1000}{60}$$

$$\Phi = 0.03 \text{ wb}$$

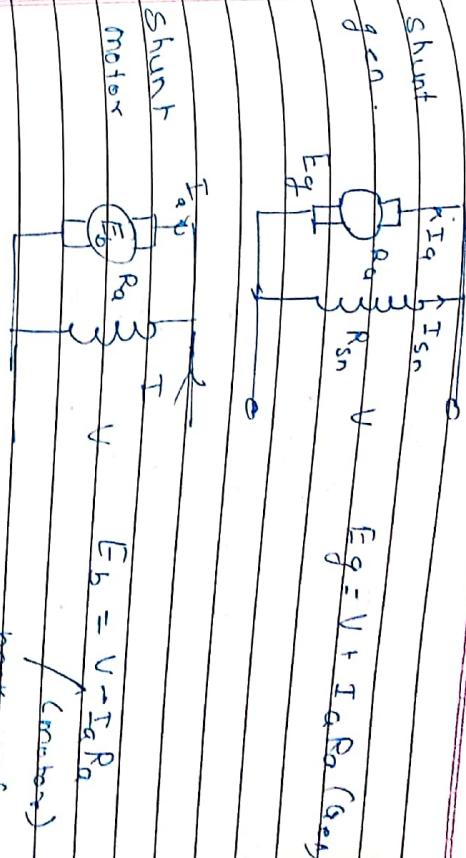

Shunt

k_I_a

I_a

T

R_s

V

E_b

I_a

R_a

E_g

I_a

T

R_s

V

E_g

I_a

T


R_s

V

E_g


I_a

T

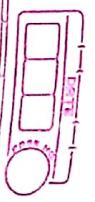



MENSI-COMPILER

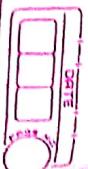

$$E_p = 220 \text{ V}$$

$$E_p = \frac{N_2}{N_1} E_o$$

$$N_2 = \frac{E_o \times N_1}{E_p}$$

$$= 60 \times 220$$

$$= 0.03 \times 200$$

$$N_2 = 50 \text{ rpm}$$

Q.2 A 200 volt DC shunt motor runs at 1000 rpm when armature current is 25 A. passing

$$\Rightarrow E_1 = 4.44 f B_m A N_1$$

$$f = 50 \text{ Hz}$$

$$N_1 = 30, N_2 = 350$$

$$A = 250 \times 10^{-4} \text{ m}^2$$

$$E_1 = 230 \text{ V}$$

$$I_s = 100 \text{ A}$$

In shunt motor $E_b \propto N$

but f is const.

$$E_{b1} = 200 - 25 \times 0.5$$

$$E_{b1} = 187.5 \text{ V}$$

$$E_{b2} = 200 - 10 \times 0.5$$

$$E_{b2} = 195 \text{ V}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2} : \frac{187.5}{195} = \frac{1000}{N_2}$$


$$\begin{aligned} \textcircled{1} \quad B_m &= \frac{E_1}{4.44 f A N_1} \\ &= \frac{230}{4.44 \times 50 \times 250 \times 10^{-4} \times 30} \\ &= \end{aligned}$$

$$i_1 = 30 \times 100$$

- A single phase 50 V transformer has 350 secondary turns of primary has 30 Net cross sectional area is 250 cm^2 , IP estimate winding is connected to 230 V, 50 Hz supply calculate
- ① Peak value of flux density in core
 - ② Voltage induced in secondary winding
 - ③ The primary current when secondary current is 100 A


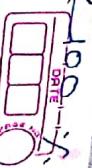
$$\eta = \frac{P_{out}}{2KVA \cos \phi} + P_i + 2^2 P_{cu}$$



2] 200 KVA, 11 KV/415 V 50 Hz transformer has 80 turns in

secondary & calculate

percentage of turns

full load secondary current

Apparent value of percentage

current considered

to be ideal

$$V_s = 11 \text{ KV}$$

$$V_p = 415 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$N_p = 80$$

$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$

$$N_s = \frac{415}{4 \times 10^3} \times 80$$

$$N_s = 10$$

To 200 KVA, 200/400 V transformer

The iron losses are 350 watt whereas core loss is 400 watt

at full load and calculate efficiency of transformer at full load

$$I_s = 481.92 \text{ A}$$

$$P_o = V_s I_s$$

$$= 11 \times 10^3 \times I_s$$

$$V_s = 2000, V_p = 200, \cos \phi = 1$$

$$I_s = 18.1818 \text{ A}$$

$$P_o = V_s I_s = 25 \text{ KVA}$$

$$\text{Full load } \rightarrow \eta = \frac{2.5 \times 10^3}{2.5 \times 10^3 + 350 + 400}$$

$$\eta_{full} = \frac{1.97087 \times 10^3}{1.97087 \times 10^3 + P_i + P_{cu}} = 97.08\%$$

~~Efficiency of Xmax~~

$$\eta = \frac{(2KVA \cos \phi)}{(2KVA \cos \phi) + 2^2 P_i + P_{cu}} \times 100$$

$$= \frac{1}{2} \times \frac{(KVA \text{ rating}) \times \cos \phi}{(2 \times (KVA \text{ rating}) \times \cos \phi) + P_i + P_{cu}}$$

$$= \frac{22}{22 + L_{load}}$$

$$P_i = V_s \text{ of load}$$

$$P_{cu} \rightarrow I_s \rightarrow \text{variable loss}$$

current is variable so Pcu

are variable as resistance

changes

1) To 200 KVA, 200/400 V transformer

The iron losses are 350 watt whereas core loss is 400 watt at full load and calculate efficiency of transformer at full load

$$I_s = 18.1818 \text{ A}$$

$$V_s = 2000, V_p = 200, \cos \phi = 1$$

$$P_o = V_s I_s = 25 \text{ KVA}$$

$$\text{Full load } \rightarrow \eta = \frac{2.5 \times 10^3}{2.5 \times 10^3 + 350 + 400}$$

$$\eta_{full} = \frac{1.97087 \times 10^3}{1.97087 \times 10^3 + P_i + P_{cu}} = 97.08\%$$

$$P_F = 200 \text{ W}$$

$$\therefore P = R_{\text{L}} I^2$$

$$R_L = P + S + \Delta P$$

$$I = P / R_L$$

$$I = \frac{P}{R_L} = \frac{200}{100} = 2 \text{ A}$$

$$Q = 500 \times 100$$

$$0.92^2 + 0.97^2 = 50 \quad \text{--- (1)}$$

at H.L

Cu loss at Half load changes

Total loss = const

$$\therefore \text{Cu loss} = \left(\frac{I_1}{I_2} \right)^2 \times \frac{R_1}{R_2} - 1$$

$$\therefore \alpha + H.L = 90^\circ$$

$$P_F = R_L I^2 + R_{\text{L}} \Delta P$$

$$\therefore Q = \frac{250}{250 + 2x + 2}$$

$$Q = (2R_{\text{L}} + R_{\text{L}}) = 2R_{\text{L}}$$

$$R_{\text{L}} = 90 \Omega$$

$$2R_{\text{L}} + (R_{\text{L}}) = 500 \Omega$$

$$\therefore \text{losses} = 500$$

$$X_{\text{max}}$$


$$0.92 + 0.225 \times 2 = 25 \quad \text{--- (2)}$$

Copper losses = $\alpha \text{ m}$

at H.L

$$\text{Total losses} = 2x + \frac{\alpha}{2}$$

~~Topic~~

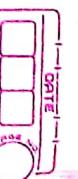

$$W/I \quad D_{ov.} = 0.75 \times 500 \\ \text{D.F.} \quad \text{0.75 transformer +}$$

$$P_{15\%} = 30.5 \text{ V}$$

$$3) \quad A \quad 10 \text{ kVA}, 50 \text{ Hz} \quad 2300/230 \text{ V} \\ \text{transformer has iron loss of } 82.2 \text{ W at full load of copper}$$

loss of 150 watt at full load
+ is supplying load having power factor of 0.8 lagging and rated voltage of 230 V and 0.8 pf + over

) at full load it is 60% of full load

$$P_{Fe} = \frac{2 \text{ kVA cost}}{\text{surface per pit} + 2 \rho_{Fe}}$$

$$Q) \quad 10 \text{ kVA} = 10 \times 10^3 \text{ VA} = 10^4 \text{ watt} \\ = 1 \times 10^4 \times 0.8 = 8000 \text{ W} \\ = 8 \times 10^4 \times 0.2 + 82.2 + 14150$$

$$P_{Fe} = 8 \times 37.17 \text{ W}$$

$$\text{Power} = 0.6 \times 10^4 \times 0.8 \\ = 6 \times 10^4 \times 0.8 + 82.2 + 14150$$

$$= 97.24 \text{ W}$$

A 400 kVA distribution X max load P.U.
load iron losses of 2.5 kwatt &
copper loss of 3.5 kw during day
night, its load cycle for 24 hrs
is as follows

6 hrs :- 300 kW at 0.8 (Day)

4 hrs :- 100 kW at 0.9 (Night)

Determine all day efficiency

Total losses will be const through
out the day

$$\text{Energy spent} = E_i = 2.5 \times 24 \text{ kWh} \\ \text{due to iron} \\ \text{losses for 24 hrs} = 60 \text{ kWh}$$

$$\text{Energy off} = (300 \times 6) + (200 \times 10) + (100 \times 6)$$


Energy spent due to Cu-loss

Q) had 1 :- 300 kW at 0.8 pf lag

$$\text{KVA supplied} = \frac{300}{0.8} = 375 \text{ KVA}$$

$$\text{Loading} = \frac{375}{400} \times 100 = 93.75 \%$$
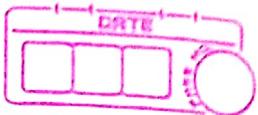
$$\therefore \text{Cu loss} = (0.9375)^2 \times 3.50 = 3.076 \text{ kW} \\ \text{for load 1 -}$$



Energy spent on Cu loss For load 1 - 3.076
= 18.46 kWh

(b) Load 2: 200kW, 0.7 pf load

$$\text{kVA} = \frac{200}{0.7} = 285.71 \text{ kVA}$$

$$\therefore \eta_2 = \frac{285.71}{400} \times 100 = 71.42\%$$

$$\begin{aligned} \text{Cu loss} &= (0.7142)^2 \times 3.5 \\ \text{For load} &= 1.785 \end{aligned}$$

$$\text{Energy spent} = 1.785 \times 10 = 17.85 \text{ kWh}$$

(c) Load 3: 100kW, 0.9 pf load

$$\text{kVA} = \frac{100}{0.9} = 111.11$$

$$\therefore \eta_3 = \frac{111.11}{400} \times 100 = 27.77$$

$$\begin{aligned} \text{Cu loss} &= (0.2777)^2 \times 3.5 \\ &= 0.2700 \end{aligned}$$

$$\text{Energy} = 0.2700 \times 4 = 1.08$$

* Total energy spent = 18.46 + 17.85 + 1.08
for copper loss (E_{Cu}) 37.4 kWh

$$E_{imp} = 60 \text{ kWh} \quad \left. \right\} \rightarrow 97.4 \text{ kWh}$$

$$\therefore \text{o/p} = 4200 \text{ kWh}$$

$$\begin{aligned} \therefore \eta &= \frac{4200}{4200 + 97.4} \times 100 \\ &= 97.7\% \end{aligned}$$